

Vibrations and waves: exercise sheet 4

Passive amplification via an LRC circuit

Consider a circuit consisting of a series connection of a resistor, inductor and capacitor. Thus circuit is driven by an alternating voltage.

The relevant differential equation is

$$L\ddot{Q} + R\dot{Q} + Q/C = V_0 \cos \omega t$$

Show that this can be reduced to the more conventional form

$$\ddot{Q} + \gamma\dot{Q} + \omega_0^2 Q = \frac{V_0}{L} \cos \omega t$$

Just divide by L and substitute ...

Obtain the steady state solution by analogy with previous work, writing your answer in terms of the variables L , C and R .

Differentiate your equation with respect to time, and hence derive an equation for the current.

$$Q = Q_0(\omega) \cos(\omega t - \delta)$$

$$Q(\omega) = \frac{V_0}{\omega \sqrt{(1/\omega C - \omega L)^2 + R^2}}$$

$$I = \dot{Q} = -\omega Q_0(\omega) \sin(\omega t - \delta)$$

$$= \frac{V_0 \sin(\omega t - \delta)}{\sqrt{(1/\omega C - \omega L)^2 + R^2}}$$

At which angular frequency will the current have maximum value?

Resonant frequency

What will be the resonant frequency and Q for $C = 8 \mu\text{F}$, $L = 0.02 \text{ H}$ and $R = 75 \Omega$?